

## Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University  
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Computing Layers

- Problems
- Algorithms
- Language
- Instruction Set Architecture
- Microarchitecture
- Circuits ←
- Devices

CS270 - Fall Semester 2014 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Combinatorial Logic

- Cascading set of logic gates

What is the truth table?

CS270 - Fall Semester 2014 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Truth Table (from circuit)

- Truth table for circuit on previous slide

A	B	C	W	X	Y	Z
0	0	0	0	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	0	0

CS270 - Fall Semester 2014 4


## Logisim Simulator

- ◆ Logic simulator: allows interactive design and layout of circuits with AND, OR, and NOT gates
- ◆ Simulator web page (linked on class web page)  
<http://ozark.hendrix.edu/~burch/logisi>
- ◆ Overview, tutorial, downloads, etc.
- ◆ Windows or Linux operating systems
- ◆ Logisim demonstration
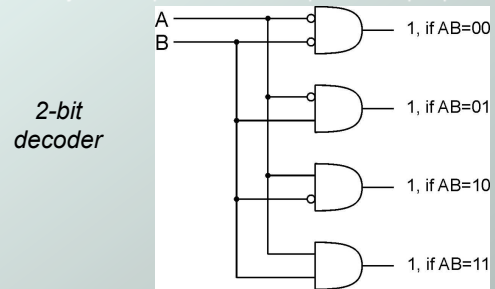
## Decoder


- ◆  $n$  inputs,  $2^n$  outputs

- exactly one output is 1 for each possible input pattern



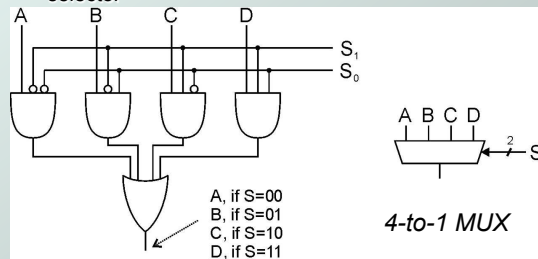
## Multiplexer (MUX)

- ◆  $n$ -bit selector and  $2^n$  inputs, one output
- output equals one of the inputs, depending on selector



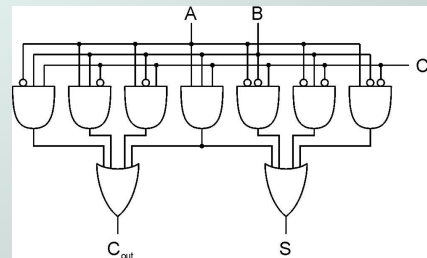
## Full Adder

- ◆ Add two bits and carry-in, produce one-bit sum and carry-out.



A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

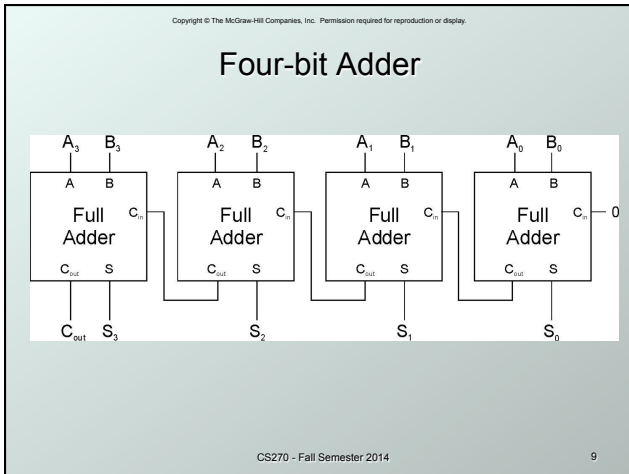

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### Logical Completeness

- Can implement **ANY** truth table with combo of AND, OR, NOT gates.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

- AND combinations that yield a "1" in the truth table.
- OR the results of the AND gates.

CS270 - Fall Semester 2014 10

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### Truth Table (to circuit)

- How do we design a circuit for this?

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

CS270 - Fall Semester 2014 11

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### Programmable Logic Array

- Front end is a input decode
- Back end selects outputs
- Not necessarily minimal circuit!
- Logic arrays are prebuilt

CS270 - Fall Semester 2014 12

## Looking Ahead: C Structures

- ◆ Useful for data structures

```
struct student
{
    char *lastName;
    char *firstName;
    Date birthDate;
    ...
};
struct student s;
s.lastname = (char *)malloc(80);
strcpy(s.lastname, "Smith");
```

CS270 - Fall Semester 2014

13

## Looking Ahead: Dynamic Memory

- ◆ Static versus dynamic memory allocation:

```
// static allocation
char name[80];
strcpy(name, "Smith");
printf("Name: %s\n", name);

// dynamic allocation
char *name = (char *)malloc(80);
strcpy(name, "Smith");
printf("Name: %s\n", name);
free(name);
```

CS270 - Fall Semester 2014

14

## Looking Ahead: String Tokens

- ◆ How to extract tokens from a string:

```
char *token = strtok(string, " \t");
while (token != null)
{
    tokens[numTokens] = (char *)
        malloc(strlen(token)+1);
    strcpy(tokens[numTokens], token);
    token = strtok(NULL, " \t");
    numTokens++;
}
```

CS270 - Fall Semester 2014

15