

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Computing Layers

- Problems
-
- Algorithms
-
- Language
-
- Instruction Set Architecture
-
- Microarchitecture
-
- Circuits
-
- Devices ←

CS270 - Spring Semester 2014 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Transistor: Building Block of Computers

- ◆ Microprocessors contain lots of transistors
 - Intel 8086 (1978): 29 thousand
 - Intel 80186 (1982): 55 thousand
 - Intel 80386 (1985): 275 thousand
 - Intel 80486 (1989): 1.1 million
 - Intel Pentium (1993): 3.1 million
 - Intel Pentium II (1998): 7.5 million
 - Intel Pentium III (2001): 45 million
 - Intel Pentium 4 (2006): 184 million
 - Intel Core 2 Duo (2006): 291 million
 - Intel Quad Core i7 (2011): 1.1 billion
 - Intel 8-core Xeon (2012): 2.3 billion

CS270 - Spring Semester 2014 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Transistor: Building Block of Computers

Logically, each transistor acts as a switch

- ◆ Combined to implement logic functions (gates)
 - AND, OR, NOT
- ◆ Combined to build higher-level structures
 - Adder, multiplexer, decoder, register, memory ...
 - Adder, multiplier ...
- ◆ Combined to build simple processor
 - LC-3

CS270 - Spring Semester 2014 4

Simple Switch Circuit

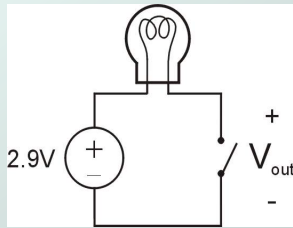


- Switch **open**:
 - Open circuit, no current
 - Light is **off**
 - V_{out} is **+2.9V**
- Switch **closed**:
 - Short circuit across switch, current flows
 - Light is **on**
 - V_{out} is **0V**

Switch-based circuits can easily represent two states: on/off, open/closed, voltage/no voltage.



n-type MOS Transistor

- MOS = Metal Oxide Semiconductor
 - two types: n-type and p-type

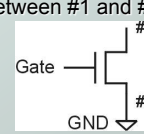- n-type
 - when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
 - when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)



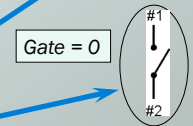
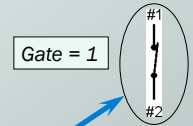
Terminal #2 must be connected to GND (0V).




p-type MOS Transistor

- p-type is **complementary** to n-type

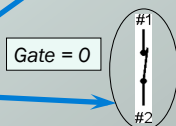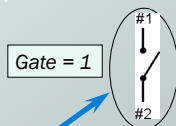
- when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)



Terminal #1 must be connected to +2.9V.

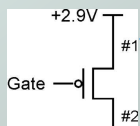


Physical Transistor

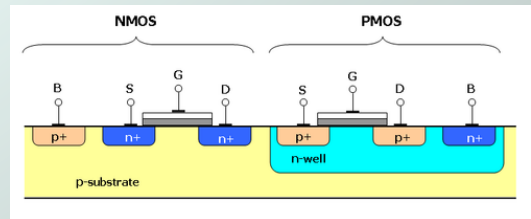


<http://en.wikipedia.org/wiki/CMOS>

Transistor Output (Ideal)

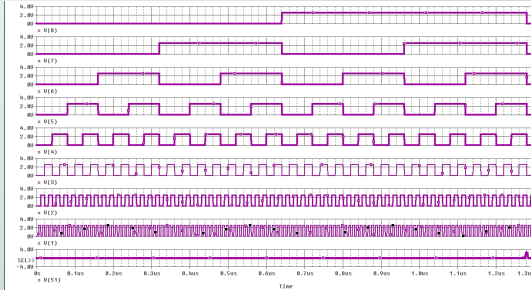

Logic analyzer view of waveforms

Transistor Output (Actual)

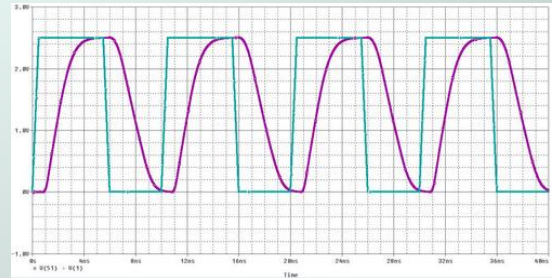

Actual waveform is not ideal!

Logic Gates

- Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.
- Digital symbols:
 - recall that we assign a range of analog voltages to each digital (logic) symbol






- assignment of voltage ranges depends on electrical properties of transistors being used
 - typical values for "1": +5V, +3.3V, +2.9V
 - from now on we'll use +2.9V

CMOS Circuit

- Complementary MOS**
- Uses both **n-type** and **p-type** MOS transistors
 - p-type
 - Attached to + voltage
 - Pulls output voltage UP when input is zero
 - n-type
 - Attached to GND
 - Pulls output voltage DOWN when input is one
- For all inputs, make sure that output is either connected to GND or to +, but not both!**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Inverter (NOT Gate)

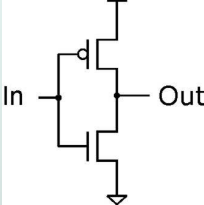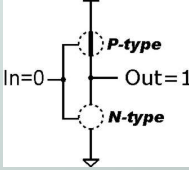
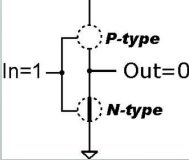
In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0

Truth table

CS270 - Spring Semester 2014 13

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

NOR Gate (OR-NO)

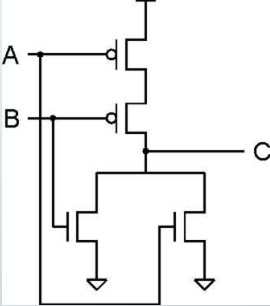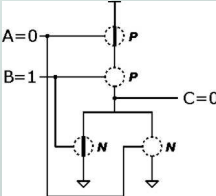A	B	C
0	0	1
0	1	0
1	0	0
1	1	0


Truth table

Note: Serial structure on top, parallel on bottom.

CS270 - Spring Semester 2014 14

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

OR Gate

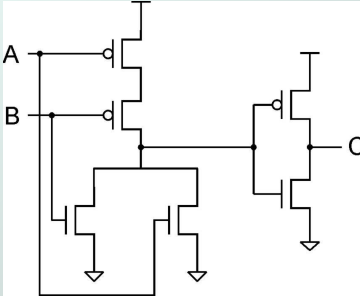

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1



Truth table

Add inverter to NOR.

CS270 - Spring Semester 2014 15

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

NAND Gate (AND-NOT)

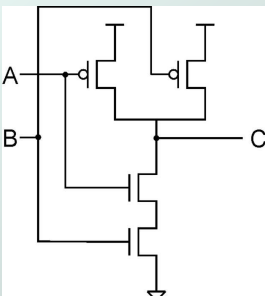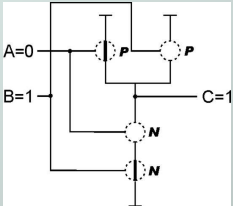A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

Note: Parallel structure on top, serial on bottom.

CS270 - Spring Semester 2014 16

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

AND Gate

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

Add inverter to NAND.

CS270 - Spring Semester 2014 17

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Basic Logic Gates

NOT: $A \rightarrow \bar{A}$

OR: $A, B \rightarrow A+B$

NOR: $A, B \rightarrow \overline{A+B}$

AND: $A, B \rightarrow AB$

NAND: $A, B \rightarrow \overline{AB}$

CS270 - Spring Semester 2014 18

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

DeMorgan's Law

- Converting AND to OR (with some help from NOT)
- Consider the following gate:

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\overline{\bar{A} \cdot \bar{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

To convert AND to OR (or vice versa), invert inputs and output.

Same as A OR B!

CS270 - Spring Semester 2014 19

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

More than 2 Inputs?

- AND/OR can take any number of inputs.
 - AND = 1 if all inputs are 1.
 - OR = 1 if any input is 1.
 - Similar for NAND/NOR.
- Can implement with multiple two-input gates, or with single CMOS circuit.

CS270 - Spring Semester 2014 20

Summary

- ◆ MOS transistors are used as switches to implement logic functions.
 - n-type: connect to GND, turn on (1) to pull down to 0
 - p-type: connect to +2.9V, turn on (0) to pull up to 1
- ◆ Basic gates: NOT, NOR, NAND
 - Logic functions are usually expressed with AND, OR, and NOT
- ◆ DeMorgan's Law
 - Convert AND to OR (and vice versa) by inverting inputs and output

Building Functions from Logic Gates

- ◆ **Combinational Logic Circuit**
 - output depends only on the current inputs
 - stateless
- ◆ **Sequential Logic Circuit**
 - output depends on the sequence of inputs (past and present)
 - stores information (state) from past inputs
- ◆ We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.