

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by Chris Wilcox, Colorado State University

Computing Layers

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

- Problems
-
- Algorithms
-
- Language
-
- Instruction Set Architecture
-
- Microarchitecture
-
- Circuits ←
-
- Devices

CS270 - Spring Semester 2014 2

Combinational vs. Sequential

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

- ◆ **Combinational Circuit**
 - does not store information, always gives the same output for a given set of inputs
 - ◆ *example*: adder always generates sum and carry, regardless of previous inputs
- ◆ **Sequential Circuit**
 - stores information, output depends on stored info (state) plus input
 - so a given input might produce different outputs, depending on the stored information
 - useful for building “memory” elements and “state machines”
 - ◆ *example*: ticket counter

CS270 - Spring Semester 2014 3

R-S Latch: Simple Storage Element

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


- ◆ R is used to “reset” or “clear” the element – set it to zero.
- ◆ S is used to “set” the element – set it to one.

- ◆ If both R and S are one, output could be either zero or one.
 - “quiescent” state -- holds its previous value
 - if a is 1, b is 0, and vice versa


CS270 - Spring Semester 2014 4

Clearing the R-S latch

 - Suppose we start with output = 1, then change R to zero.




Output changes to zero.

 


Then set R=1 to "store" value in quiescent state.

Setting the R-S Latch

 - Suppose we start with output = 0, then change S to zero.



Output changes to one.

 


Then set S=1 to "store" value in quiescent state.

R-S Latch Summary

- R = S = 1**
 - hold current value in latch
- S = 0, R=1**
 - set value to 1
- R = 0, S = 1**
 - set value to 0
- R = S = 0**
 - both outputs equal one
 - final state determined by electrical properties of gates
 - Don't do it!**


Gated D-Latch

 - Two inputs: D (data) and WE (write enable)
 - when **WE = 1**, latch is set to **value of D**
 - S = NOT(D), R = D
 - when **WE = 0**, latch holds **previous value**
 - S = R = 1



Register

 - A register stores a multi-bit value.
 - We use a collection of D-latches, all controlled by a common WE.



Representing Multi-bit Values

- Number bits from right (0) to left (n-1)
 - just a convention -- could be left to right, but must be *consistent*
- Use brackets to denote range:
 - $D[l:r]$ denotes bit l to bit r , from *left to right*

$$A = \overset{15}{0}1010011010101\overset{0}{1}$$

$$A[14:9] = 101001$$

$$A[2:0] = 101$$

- May also see $A\langle 14:9 \rangle$, especially in hardware block diagrams.


Memory

- Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.


Address Space:
number of locations
(usually a power of 2)

$k = 2^n$
locations

 Addressability:
number of bits per location
(e.g., byte-addressable)




$2^2 \times 3$ Memory

 

More Memory Details

- ◆ Not the way actual memory is implemented!
 - fewer transistors, denser, relies on electrical properties
- ◆ But the logical structure is very similar.
 - address decoder, word select line, word write enable
- ◆ Random Access Memory: 2 different types
 - **Static RAM** (SRAM)
 - ◆ fast, used for caches, maintains data when powered
 - **Dynamic RAM** (DRAM)
 - ◆ slower but denser, storage decays, must be refreshed
- ◆ Non-Volatile Memory: **ROM, PROM, Flash**

 

Memory Bandwidth

- ◆ Bandwidth is the rate at which memory can be read or written by the processor.
- ◆ Approximately equal to the memory bus size times the speed at which the memory is clocked.
- ◆ Examples of bandwidth (from Wikipedia):
 - Phone line, Modem, up to 5.6KB/s
 - Digital subscriber line, ADSL, up to 128KB/s
 - Wireless networking, 802.11g, up to 17.5MB/s
 - Peripheral connection, USB 2.0, 60MB/s
 - Digital video, HDMI, up to 1.275GB/s
 - Computer bus, PCI Express, up to 25.6GB/s
 - Memory chips, SDRAM, up to 52GB/s

Looking Ahead: C Arrays

- ◆ Similar to Java arrays

```
// integer array
int iArray[3] = {1,2,3};
printf("iArray[2]: %d", iArray[2]);

// float array
float fArray[2] = {0.1f,0.2f};
printf("fArray[1]: %f", fArray[1]);

// character array
char cArray[4] = {'a','b','c','d'};
printf("cArray[3]: %c", cArray[3]);
```

Looking Ahead: C Strings

- ◆ Array of chars with null termination

```
// string: static allocation
char *string1 = "Hello World\n";
printf("string1: %s", string1);

// string: dynamic allocation
char *string2 = (char *)malloc(13);
strcpy(string2, "Hello World\n");
```

Note that the programmer is responsible for making sure string has enough memory!

Looking Ahead: C Arrays and C Pointers

- Array name is a pointer to array

```
int iArray[2] = {1234, 5678};

printf("iArray[0]: %d", iArray[0]);
printf("iArray[1]: %d", iArray[1]);
printf("&iArray[0]: %x", &iArray[0]);
printf("&iArray[1]: %x", &iArray[1]);
printf("iArray: %x", iArray);
iArray[2] = 0; // out of bounds!
```

Looking Ahead: C Functions

- Can pass by value or reference

```
// by value (copies value)
float f1(int i, float f);
// by reference (copies pointer)
float f2(float *f);
```

- Function cannot change values passed by value

```
f1: i = 10; // changes the copy
```

- Function can change values passed by reference

```
f2: *f = 1.2; // changes actual value
```