

# CS470 Spring 2008

## Homework Assignment 1

Due Feb. 12, 2008

### Problem 1:

a. The truth table for a combinational circuit is given below with the inputs A, B and C and the outputs X, Y and Z. Obtain minimized expressions for X, Y and Z in sum-of-products form.

| A | B | C | X | Y | Z |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | x | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 |

| A \ B C | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 0       |    |    |    |    |
| 1       |    |    |    |    |

X=

| A \ B C | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 0       |    |    |    |    |
| 1       |    |    |    |    |

Y=

| A \ B C | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 0       |    |    |    |    |
| 1       |    |    |    |    |

Z=

c. Give a logic diagram for both using AND gates, OR gates and inverters. Verify the design using Logisim (see lab assignment)

d. Implement the above function as a PLA. Minimize the number of product terms. Show the table as well as the PLA diagram.

**Problem 2:** Obtain minimized SOP expressions.

AB\CD    00   01   11   10

|    |   |   |   |   |
|----|---|---|---|---|
| 00 |   |   |   |   |
| 01 | 1 |   |   | 1 |
| 11 | 1 | 1 | 1 | 1 |
| 10 |   | 1 |   |   |

AB\CD    00   01   11   10

|    |   |   |   |   |
|----|---|---|---|---|
| 00 | x |   |   | 1 |
| 01 |   | 1 | 1 |   |
| 11 |   |   | 1 |   |
| 10 | 1 |   |   | 1 |

a\bc    00   01   11   10

|   |   |   |  |   |
|---|---|---|--|---|
| 0 | 1 | x |  | 1 |
| 1 | 1 | 1 |  |   |

**Problem 3:** Answer questions B.7 and B.9 from the text (Appendix B on CD). Minimize the PLA. (Use extra paper as needed).