

## Testing Sequential Circuits

- **Test for**
  - **Functionality**
  - **Timing (components too slow, too fast, not synchronized)**
- **Parts:**
  - **Combinational logic:** faults: stuck 0/1, delay
  - **Flip-flops:** faults: input, output stuck 0/1, delay  
no latch 0/1 capability
- **Cases:**
  - **Without feedback**
  - **With feedback**

Our work

Our work




September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

1
 
## Testing Sequential circuits without feedback



1. **Generate test vectors for the combinational circuit.**
2. **Place a vector in A**
3. **Examine response in B**
4. **2,3 can be done using**
  - a. **Machine instructions**
  - b. **Microinstructions**
  - c. **Specialized hardware**




September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

2

## BIST (Built-in self-test)

 

ALFSR: autonomous linear feedback shift register.  
 Better generators include our antirandom test generator.

- Generator generates pseudorandom vectors. Often an ALFSR.
- Signature analyzer compresses all successive responses into a signature. Usually an LFSR.
- Compared with known good signature.
- Aliasing probability: prob. that a bad circuit can result in good signature. Very small.
- BILBO: PIPO, SA functions




September 25, 2000

Fault Tolerant Computing  
 ©Y.K. Malaiya

3

## Sequential Circuits with feedback

 

Software testing correspondence?

- Example: processor control unit
  - Input: status, opcode
  - Output: control lines
- Structural testing:
  - How to obtain a desired (x,y) vector
  - How to propagate error
- Functional testing:
  - Prove presence of all states
  - Prove all transitions/outputs correct





September 25, 2000

Fault Tolerant Computing  
 ©Y.K. Malaiya

4

## Sequential Circuits with feedback: Approaches

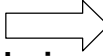 - Consider the sequential behavior: 
- Design for testability: feedback-less during testing



- Scan Design: modes
  - Normal: parallel in/out
  - Test: serial in/out
- Sequence
  - Scan a vector: test mode
  - Latch response: normal mode
  - Scan response out: test mode
- Chain too long
  - Multiple chain
  - Partial scan





September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

5

## D- Algo: Sequential Circuits

Equivalent iterative array model:

 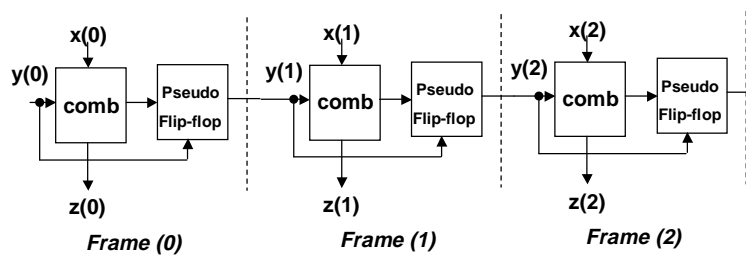

Q	Din	Q+
0	0	0
0	1	1
1	0	0
1	1	1

Pseudo-flipflop is a combinational block.



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

6

## D- Algo.: Seq Circuit Extension

- One time-frame for each clock-period. Converts problem to combinational. Only  $4^n$  distinct states possible (boolean values 0,1, D,  $\bar{D}$ ).
- Assume faults in the combinational logic only. ?
- Assume initial state given. ?
- Procedure: Get iterative array model, initial state
  - D-algo. to drive D or  $\bar{D}$  towards an output  $z(k)$
  - Terminate when  $\left\{ \begin{array}{l} \text{D or } \bar{D} \text{ at an output.} \\ \text{a state is repeated.} \\ \text{when } k > 4^n. \end{array} \right.$

$n = \#$  of flipflops





September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

? 7

## Seq D- Algo: Example

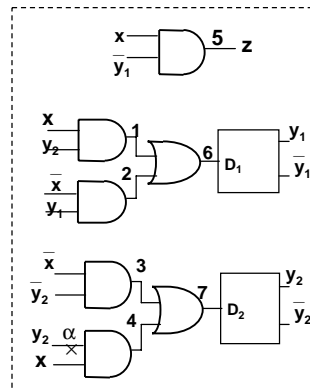 

- Start: fault  $\alpha$  s-a-1, initial state  $y_1, y_2 = (0,0)$
- Time frame 0: Since  $y_2$  already 0, line  $\alpha = \bar{D}$ 
  - For 4=  $\bar{D}$  need  $x(0)=1$
  - Since 3=0 already,  $D_2 = \bar{D}$ .
  - Also  $D_1=0$
  - Next state  $Y(1)=(0, \bar{D}), z(0)=1$



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

8

### Seq D-Algo: Ex (pt2)

- **Time frame 0:**
  - Next state  $Y(1)=(0, \bar{D})$ ,  $z(0)=1$
- **Time frame 1:** error can not yet be propagated to  $z$ .
- For  $D_1 = \bar{D}$  need  $x(1)=1$ . Gives  $D_2 = \bar{D}$ .  $Y(2)=(\bar{D}, \bar{D})$ ,
- **Time frame 2:** Since  $\bar{y}_1=D$ , choosing  $x(2)=1$  gives  $z=D$ .
- **Answer:** Test sequence  $(1,1,1)$  for initial state  $(0,0)$ .

September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

9

## Initialization Problem

- **Power-up: state undefined**
- **How to get FSM in a known state?**
  1. Applying an input sequence
  2. Resetting to an initial state
- **Resetting always used in practice**
  - using a reset/clear line
  - **Computers: power-on sequence to initialize PC, SP, interface registers etc.**
- **Problem with reset mechanism: highly testable**
  - Hence we can neglect it

September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

10

## Functional Testing of FSMs

- **Given:** state table **Objective:** confirm it is obeyed
- **Approaches:**
  1. **Only outputs observable:** “*Checking sequence*”
    - a. Prove all states exist
    - b. For all inputs for each state, these are correct
      - Next state
      - Outputs
  - Complex and lengthy (*we’ll skip it for now*)
- 2. **State observable:**
  1. Much easier
  2. *Euler path*, if it exists, can minimize testing



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

11

## Semiconductor RAMs



- **Types:** Static (cell is flip-flop), dynamic (charged capacitor)
- **Organization:** assume  $m$  address lines, assume 1 bit wide chip
- **External:** words  $\times$  bits/word =  $2^m \times 1$
- **Internal:**  $m=r+q$ 
  - $r$  lines for word-line selection
  - $q$  lines for bit-line selection



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

12

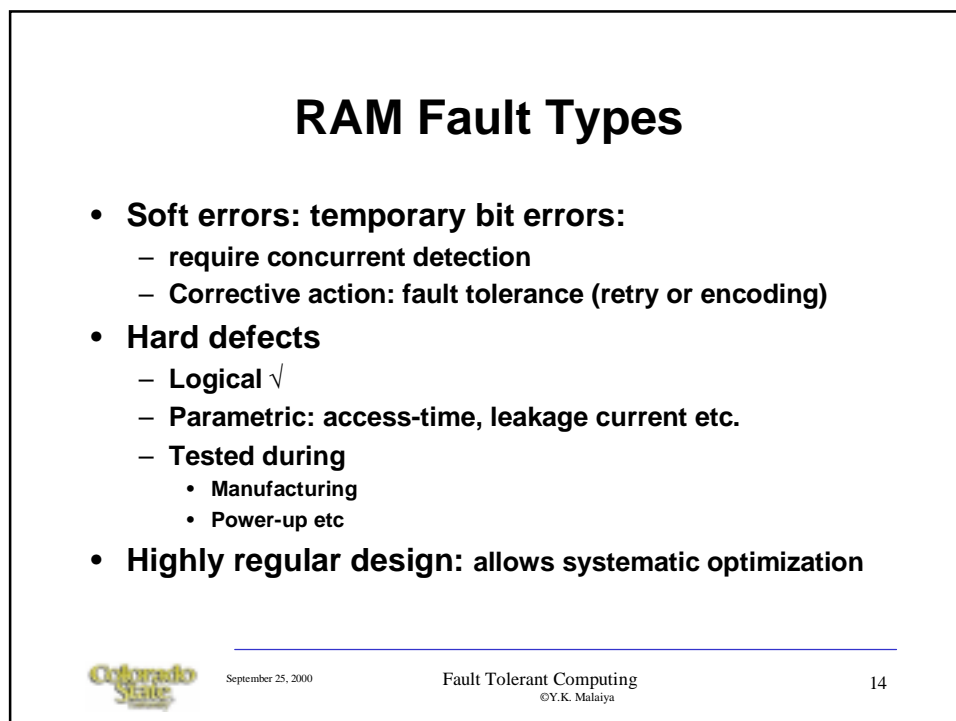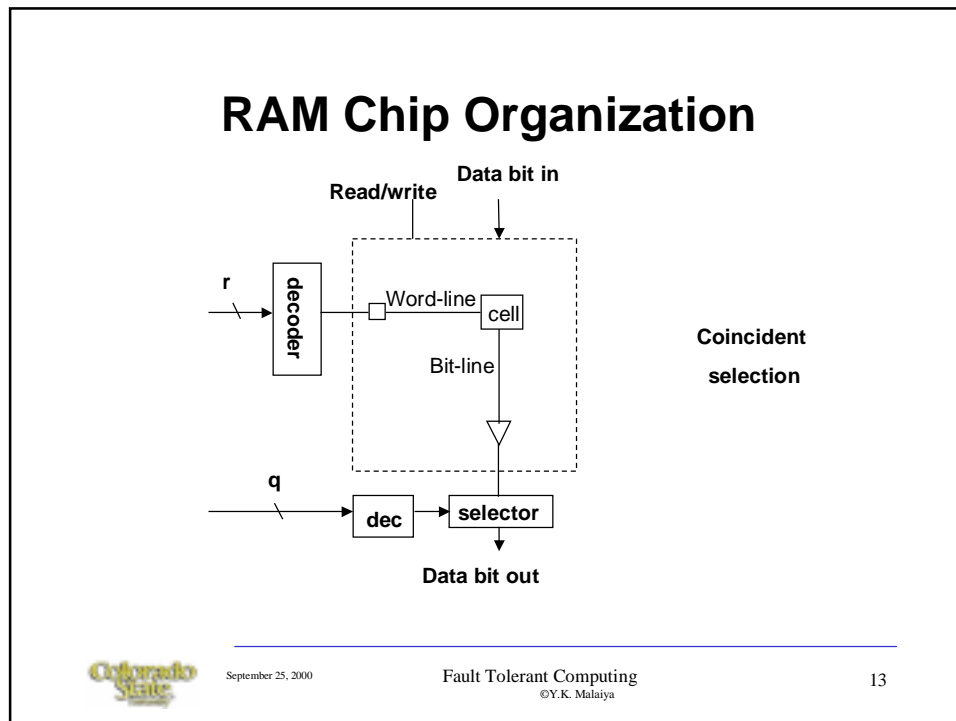

## Functional Fault Model By Abraham, Reddy etc

- **One or more cells stuck-at 0 or 1.**
  - Defects in cells
  - Read/write electronics stuck-at 0/1
  - Decoding faults
- **One or more cells fail to do  $0 \rightarrow 1$  or  $1 \rightarrow 0$ .**
  - Defects in cells
- **One or more pair of cells “coupled”**
  - $i, j$  coupled=  $0 \rightarrow 1$  or  $1 \rightarrow 0$  transition of  $i$  changes the state of  $j$  (not necessarily vice versa)
  - Decoding faults, read/write electronics coupling
- **More than one cells accessed during a read or write**
  - Decoding faults





September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

15
  
## RAM Testing: “March”

- **Step 1: Write all 0’s.**
- **Step 2: For  $i=0, \dots, n-1$  do**  
 Read  $c_i (=0)$   
 $c_i \leftarrow 1$   
 Read  $c_i (=1)$
- **Step 3: For  $i=n-1, \dots, 0$  do**  
 Read  $c_i (=1)$   
 $c_i \leftarrow 0$   
 Read  $c_i (=0)$
- **Step 4: Repeat steps 1-3 for complementary pattern.**



**Complexity:  $12n$**



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

16

## Testing for Coupling

- **To test for coupling between all cell pairs (i,j)**
  - Test bit i
  - Test bit j
  - Do some sequence of read, write operations for i & j
  - Repeat for all i
  - Repeat for all j
- **Complexity:**
  - All i and j:  $\text{const} \times n \times n = k \times n^2$
  - Same row & column only:  $k \times n \times (2\sqrt{n}) = k \times n^{1.5}$
- **Careful sequencing can reduce complexity**
  - Suk & Reddy's test satisfies fault model with 14n.



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

17

## Testing Complex Systems

- **Approach:**
  - Assume a fault model for each *component*
  - Assume a system model that takes into account interaction of components
- **Device a testing strategy such that these are adequately tested**
  - each individual component
  - Interaction of components
- **A component may be a**
  - Physical component
  - Segment of the functionality




September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

18

## Incremental Testing

 

- **Partition into layers** such that layer  $i$  can be exercised using only layers  $0, \dots, i-1$ .
- **Test components in each layer in the sequence  $L_0, L_1, \dots, L_n$ .**
- **Layering may require**
  - Assumptions
  - Disabling feedback during testing
- **Proofs of complete coverage can be constructed.**
- **Fault isolation can be done.**



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

19

## Incremental testing: Example: Processor Based systems

- **Self-test processor:**
  - Basic instructions
  - Addressing modes
  - Complex instructions
- **Test Memory system and buses using processor**
- **Test I/O devices/ports**
- **Test peripheral devices**
- **Test software integrity**



September 25, 2000

Fault Tolerant Computing  
©Y.K. Malaiya

20