

## Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University  
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Computing Layers

- Problems
- 
- Algorithms
- 
- Language
- 
- Instruction Set Architecture
- 
- Microarchitecture
- 
- Circuits
- 
- Devices ←


CS270 - Fall Semester 2015 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Transistor: Building Block of Computers

- Microprocessors contain lots of transistors
- Intel 8086 (1978): 29 thousand
- Intel 80186 (1982): 55 thousand
- Intel 80386 (1985): 275 thousand
- Intel 80486 (1989): 1.1 million
- Intel Pentium (1993): 3.1 million
- Intel Pentium II (1998): 7.5 million
- Intel Pentium III (2001): 45 million
- Intel Pentium 4 (2006): 184 million
- Intel Core 2 Duo (2006): 291 million
- Intel Quad Core i7 (2011): 1.1 billion
- Intel 8-core Xeon (2012): 2.3 billion


CS270 - Fall Semester 2015 3

 

## Transistor: Building Block of Computers

- Logically, each transistor acts as a switch
- Combined to implement logic functions (gates)
  - AND, OR, NOT
- Combined to build higher-level structures
  - Multiplexer, decoder, register, memory ...
  - Adder, multiplier ...
- Combined to build simple processor
  - LC-3

## Simple Switch Circuit

 



- Switch **open**:
  - Open circuit, no current
  - Light is **off**
  - $V_{out}$  is **+2.9V**
- Switch **closed**:
  - Short circuit across switch, current flows
  - Light is **on**
  - $V_{out}$  is **0V**

*Switch-based circuits* can easily represent two states: on/off, open/closed, voltage/no voltage.
  
## n-type MOS Transistor

- MOS = Metal Oxide Semiconductor
  - two types: n-type and p-type
- n-type
  - when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
  - when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)



Terminal #2 must be connected to GND (0V).




## p-type MOS Transistor

- p-type is *complementary* to n-type
  - when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
  - when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)

Terminal #1 must be connected to +2.9V.

  


## Physical Transistor

 


<http://en.wikipedia.org/wiki/CMOS>

## Transistor Output (Ideal)

 

Logic analyzer view of waveforms

## Transistor Output (Actual)

 

Actual waveform is not ideal!

## Propagation Delay

- ◆ Each gate has a propagation delay, typically fraction of a nanosecond ( $10^{-9}$  sec).
- ◆ Delays accumulate depending on the chain of gates the signals have to go through.
- ◆ Clock frequency of a processor is determined by the delay of the longest combinational path between storage elements, i.e. cycle time.

## Logic Gates

- Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.
- Digital symbols:
  - recall that we assign a range of analog voltages to each digital (logic) symbol




- assignment of voltage ranges depends on electrical properties of transistors being used
  - typical values for "1": +5V, +3.3V, +2.9V
  - from now on we'll use +2.9V

## CMOS Circuit


- Complementary** MOS
- Uses both **n-type** and **p-type** MOS transistors
  - p-type
    - Attached to + voltage
    - Pulls output voltage UP when input is zero
  - n-type
    - Attached to GND
    - Pulls output voltage DOWN when input is one
- For all inputs, make sure that output is either connected to GND or to +, but not both!**

## Inverter (NOT Gate)

 

In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0

**Truth table**

 

## Logical Operation: OR and NOR

A	B	OR
0	0	0
0	1	1
1	0	1
1	1	1

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Inputs: 2 or more



Output=A+B




Output= $\overline{A+B}$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


## AND and NAND

A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

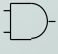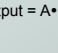
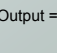
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0



Inputs: 2 or more



Output =  $A \cdot B$






Output =  $\overline{A \cdot B}$

CS270 - Fall Semester 2015

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## NOR Gate (OR-NOT)

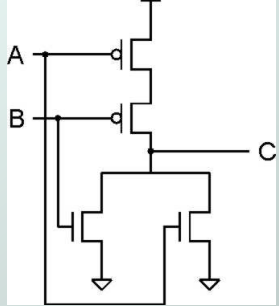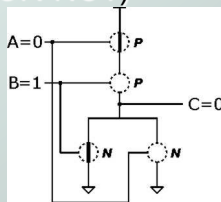A	B	C
0	0	1
0	1	0
1	0	0
1	1	0


Truth table

Note: Serial structure on top, parallel on bottom.

CS270 - Fall Semester 2015

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## OR Gate

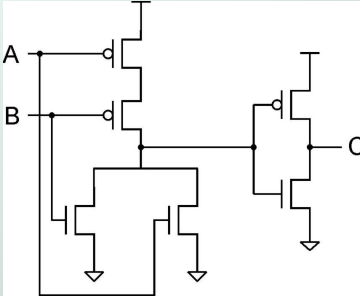

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1



Truth table

Add inverter to NOR.

CS270 - Fall Semester 2015

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## NAND Gate (AND-NOT)

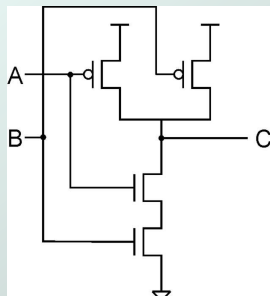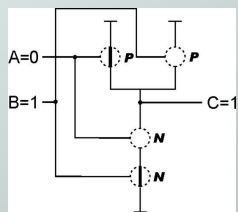A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

Note: Parallel structure on top, serial on bottom.

CS270 - Fall Semester 2015

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### AND Gate

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

**Truth table**

Add inverter to NAND.

CS270 - Fall Semester 2015 21

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### Basic Logic Gates

NOT:  $A \rightarrow \bar{A}$

OR:  $A, B \rightarrow A+B$

NOR:  $A, B \rightarrow \overline{A+B}$

AND:  $A, B \rightarrow AB$

NAND:  $A, B \rightarrow \overline{AB}$

CS270 - Fall Semester 2015 22

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### Boolean Algebra

$x$  AND  $0 = 0$        $x$  AND  $1 = x$        $x$  AND  $\bar{x} = 0$   
 $x \cdot 0 = 0$        $x \cdot 1 = x$        $x \cdot \bar{x} = 0$

$x$  OR  $0 = x$        $x$  OR  $1 = 1$        $x$  OR  $\bar{x} = 1$   
 $x + 0 = x$        $x + 1 = 1$        $x + \bar{x} = 1$

**Remember Identify, Domination, Negation Laws from Logic!**

CS270 - Fall Semester 2015

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

### Boolean Algebra Laws

- ◆ Commutative
  - $A+B = B+A$
  - $A \cdot B = B \cdot A$
- ◆ Associative
  - $A+(B+C)=(A+B)+C = A+B+C$
  - $A \cdot (B \cdot C)=(A \cdot B) \cdot C = ABC$
- ◆ Distributive
  - $A \cdot (B+C)=A \cdot B+A \cdot C$
  - $A+(B \cdot C)=(A+B) \cdot (A+C)$

CS270 - Fall Semester 2015

## Some Useful Identities for simplification

◆  $\overline{AB} + AB = A$


Proof:  $\overline{AB} + AB = \overline{A(B+B)}$  // **Distributive Law**  
 $= A(T)$  // **Negation Law**  
 $= A$  // **Identity Law**

◆  $A + AB = A$

Proof:  $A + AB = A(1+B)$  // **Distributive Law**  
 $= A(1)$  // **Domination Law**  
 $= A$  // **Identity Law**
 
## DeMorgan's Law

- ◆ Converting AND to OR (with some help from NOT)
- ◆ Consider the following gate:




A	B	$\overline{A}$	$\overline{B}$	$\overline{A \cdot B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

To convert AND to OR  
(or vice versa),  
invert inputs and output.

Same as A OR B!
 
## More than 2 Inputs?

- ◆ AND/OR can take any number of inputs.
  - AND = 1 if all inputs are 1.
  - OR = 1 if any input is 1.
  - Similar for NAND/NOR.
- ◆ Can implement with multiple two-input gates, or with single CMOS circuit.



## Summary

- ◆ MOS transistors are used as switches to implement logic functions.
  - n-type: connect to GND, turn on (1) to pull down to 0
  - p-type: connect to +2.9V, turn on (0) to pull up to 1
- ◆ Basic gates: NOT, NOR, NAND
  - Logic functions are usually expressed with AND, OR, and NOT
- ◆ DeMorgan's Law
  - Convert AND to OR (and vice versa) by inverting inputs and output

## Building Functions from Logic Gates

- ◆ **Combinational Logic Circuit**
  - output depends only on the current inputs
  - stateless
- ◆ **Sequential Logic Circuit**
  - output depends on the sequence of inputs (past and present)
  - stores information (state) from past inputs
- ◆ We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.