

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Computing Layers

- Problems
-
- Algorithms
-
- Language
-
- Instruction Set Architecture
-
- Microarchitecture
-
- Circuits ←
-
- Devices

CS270 - Fall Semester 2015 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Combinatorial Logic

- Cascading set of logic gates

What is the truth table?

CS270 - Fall Semester 2015 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Truth Table (from circuit)

- Truth table for circuit on previous slide

| A | B | C | W | X | Y | Z |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 |


CS270 - Fall Semester 2015 4

Logisim Simulator

- ◆ Logic simulator: allows interactive design and layout of circuits with AND, OR, and NOT gates
- ◆ Simulator web page (linked on class web page) <http://ozark.hendrix.edu/~burch/logisi>
- ◆ Overview, tutorial, downloads, etc.
- ◆ Windows or Linux operating systems
- ◆ Logisim demonstration


Decoder

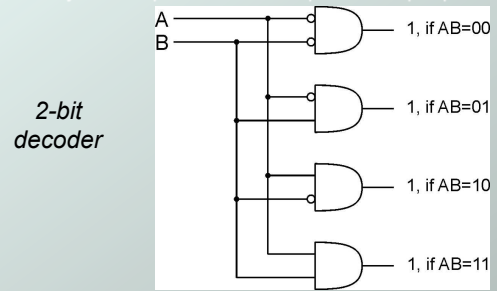- ◆ n inputs, 2^n outputs
 - exactly one output is 1 for each possible input pattern




Multiplexer (MUX)

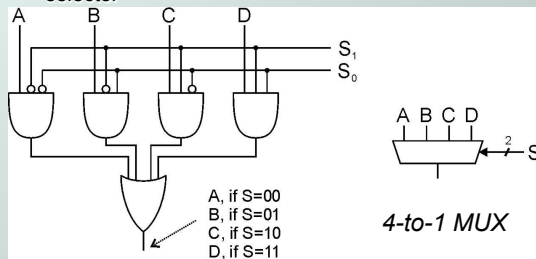
- ◆ n -bit selector and 2^n inputs, one output
 - output equals one of the inputs, depending on selector



Full Adder

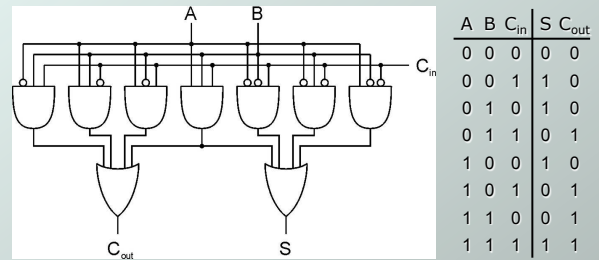- ◆ Add two bits and carry-in, produce one-bit sum and carry-out.



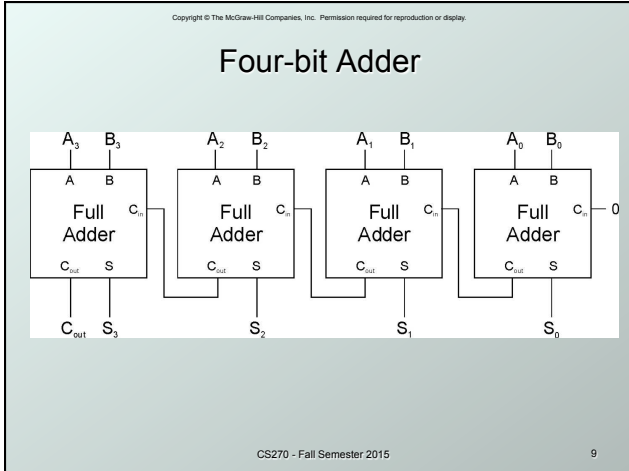

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Logical Completeness

- Can implement **ANY** truth table with combo of AND, OR, NOT gates.

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

- AND combinations that yield a "1" in the truth table.
- OR the results of the AND gates.

CS270 - Fall Semester 2015 10

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Truth Table (to circuit)

- How do we design a circuit for this?

| A | B | C | X | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

CS270 - Fall Semester 2015 11

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Programmable Logic Array

- Front end is decoder for inputs
- Back end defines the outputs
- Any truth table can be built
- Not necessarily minimal circuit!


Requires (at least) ten gates.

CS270 - Fall Semester 2015 12

Circuit Minimization

- Gate array design has one unused AND gate.
- Boolean logic lets us reduce even further:

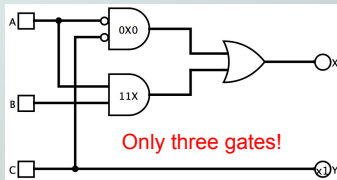- $X = \overline{A}BC + A\overline{B}C + ABC + ABC = \overline{A}C + AB$
- $Y = \overline{A}BC + \overline{A}BC + ABC + ABC = C$



| A | B | C | X | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Looking Ahead: C Structures

- Useful for data structures

```

struct student
{
    char *lastName;
    char *firstName;
    Date birthDate;
    ...
};
struct student s;
s.lastName = (char *)malloc(80);
strcpy(s.lastName, "Smith");
    
```

Looking Ahead: Dynamic Memory

- Static versus dynamic memory allocation:

```

// static allocation
char name[80];
strcpy(name, "Smith");
printf("Name: %s\n", name);

// dynamic allocation
char *name = (char *)malloc(80);
strcpy(name, "Smith");
printf("Name: %s\n", name);
free(name);
    
```

Looking Ahead: String Tokens

- How to extract tokens from a string:

```

char *token = strtok(string, " \t");
while (token != null)
{
    tokens[numTokens] = (char *)
        malloc(strlen(token)+1);
    strcpy(tokens[numTokens], token);
    token = strtok(NULL, " \t");
    numTokens++;
}
    
```