## CS270 Homework Assignment 3 (HW3)

Homework and programming assignments are to be done individually.

Instructions: Design a Logisim circuit that implements the state machine shown below:



Here are a few notes that may help you:

- What is the sequence of bits that is detected by this state machine?
- State should be stored in D-latches, how many do you need?
- The truth table is combinational logic similar to what you have already done.
- You must use a D-latch the output, since it's on a transition.
- Optimization is allowed and encouraged, the fewer gates the better!
- Why are there only 10 rows in the truth table instead of  $2^4 = 16$ ?

Current State	Input	Output	Next State
000	0	0	000
000	1	0	001
001	0		
001	1		
010	0		
010	1		
011	0		
011	1		
100	0		
100	1		

Create a Logisim circuit called HW3.circ and turn it in to the RamCT dropbox. Also, create HW3.pdf, with an image of the circuit exported from Logisim, and the following questions & answers, and turn it in to the same dropbox:

- 1. How did you represent the current state? A binary number, a line per state, or something else?
- 2. How did you label the lines that represent the current state?
- 3. How did you label the input?
- 4. How did you label the clock?
- 5. How did you label the reset line?
- 6. How did you label the output?