

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Computing Layers

Problems

Algorithms

Language

Instruction Set Architecture

Microarchitecture

Circuits ←

Devices

CS270 - Fall Semester 2016 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Combinational Logic

- Cascading set of logic gates

What is the truth table?

CS270 - Fall Semester 2016 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Truth Table (from circuit)

- Truth table for circuit on previous slide

A	B	C	W	X	Y	Z
0	0	0	0	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	0	0


CS270 - Fall Semester 2016 4

Logisim Simulator

- Logic simulator: allows interactive design and layout of circuits with AND, OR, and NOT gates
- Simulator web page
<http://www.cburch.com/logisim/>
- Overview, tutorial, downloads, etc.
- Windows or Linux operating systems
- Logisim demonstration


Decoder

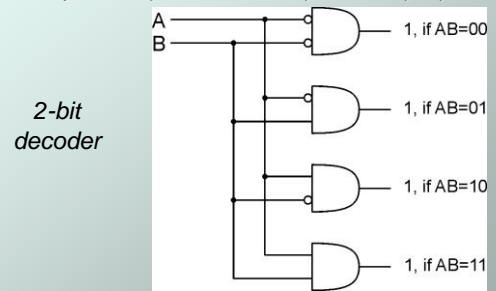- n inputs, 2^n outputs
 - exactly one output is 1 for each possible input pattern




Multiplexer (MUX)

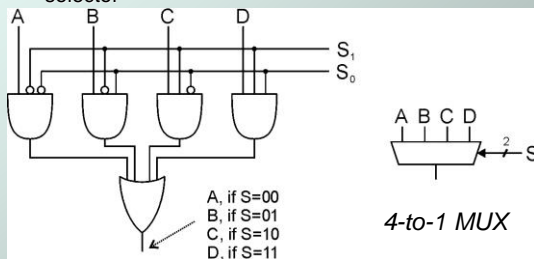- n -bit selector and 2^n inputs, one output
 - output equals one of the inputs, depending on selector




Full Adder

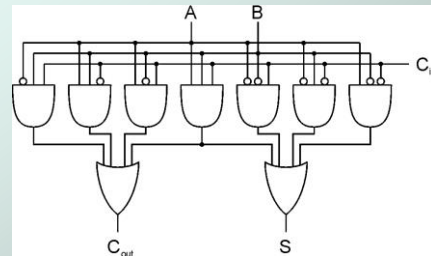- Add two bits and carry-in, produce one-bit sum and carry-out.



A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Four-bit Adder

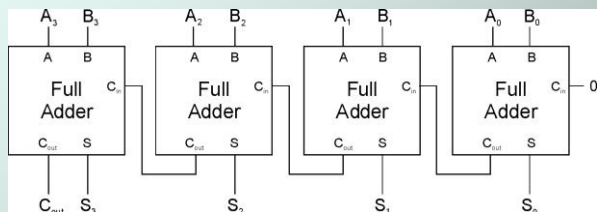

Logical Completeness

- Can implement ANY truth table with combo of AND, OR, NOT gates.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

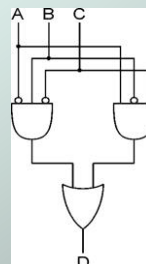

- AND combinations that yield a "1" in the truth table.
- OR the results of the AND gates.


Truth Table (to circuit)

- How do we design a circuit for this?

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

Programmable Logic Array

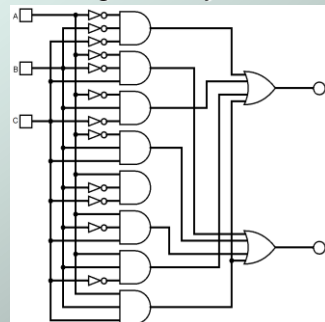- Front end reacts to specific inputs
- Back end defines the outputs
- Any truth table can be built
- Not necessarily minimal circuit!



Requires (at least) ten gates.