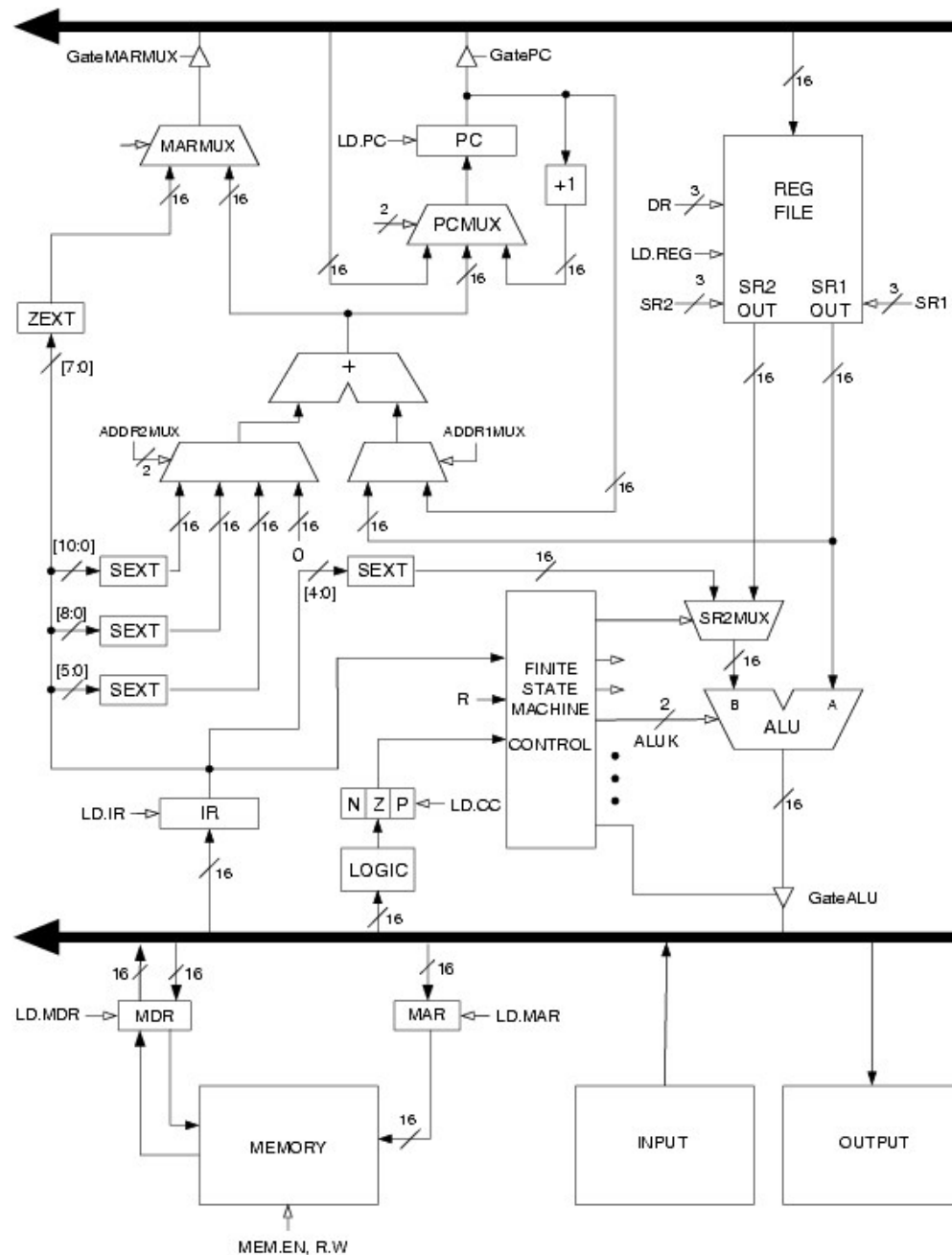


The Microarchitecture of the LC-3

LC-3 Data Path Revisited

Now Registers and
Memory



From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-3 on next slide.

Combinational Logic


- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

LC-3 Control Architecture

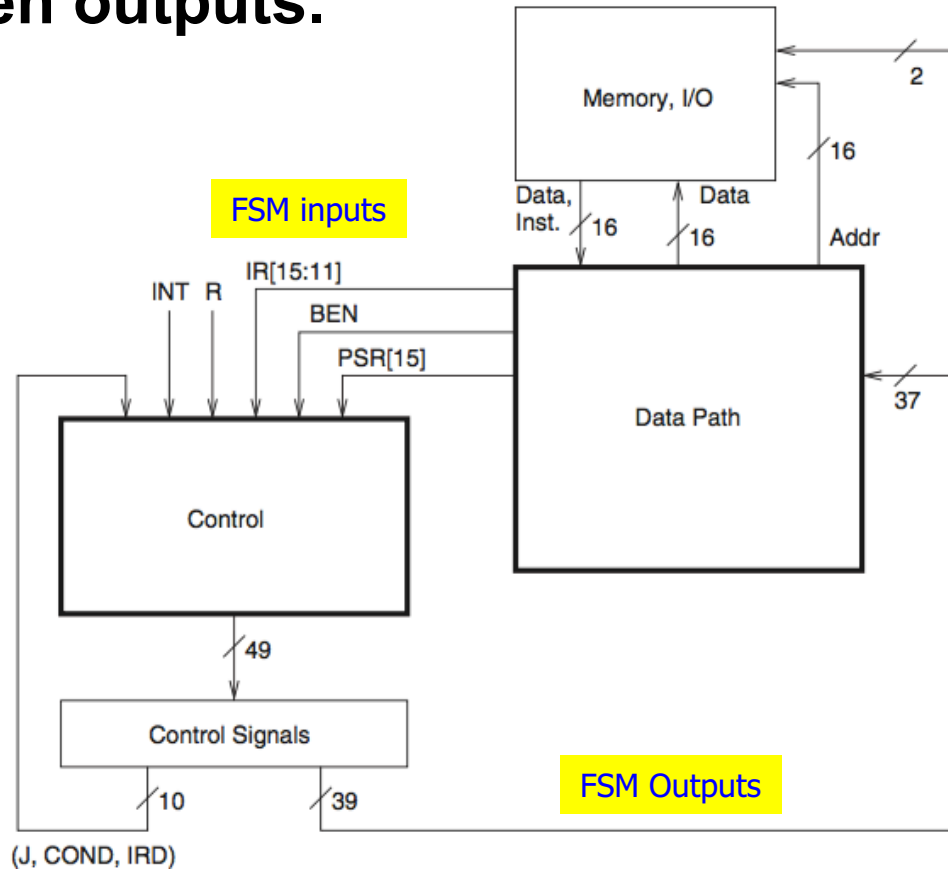Control FSM: Design a FSM with given outputs.



Signal Name	Signal Values	
LD.MAR/1:	NO, LOAD	
LD.MDR/1:	NO, LOAD	
LD.IR/1:	NO, LOAD	
LD.BEN/1:	NO, LOAD	
LD.REG/1:	NO, LOAD	
LD.CC/1:	NO, LOAD	
LD.PC/1:	NO, LOAD	
LD.Priv/1:	NO, LOAD	
LD.SavedSSP/1:	NO, LOAD	
LD.SavedUSP/1:	NO, LOAD	
LD.Vector/1:	NO, LOAD	
GatePC/1:	NO, YES	
GateMDR/1:	NO, YES	
GateALU/1:	NO, YES	
GateMARMUX/1:	NO, YES	
GateVector/1:	NO, YES	
GatePC-1/1:	NO, YES	
GatePSR/1:	NO, YES	
GateSP/1:	NO, YES	
PCMUX/2:	PC+1 BUS ADDER	;select pc+1 ;select value from bus ;select output of address adder
DRMUX/2:	11.9 R7 SP	;destination IR[11:9] ;destination R7 ;destination R6
SR1MUX/2:	11.9 8.6 SP	;source IR[11:9] ;source IR[8:6] ;source R6
ADDR1MUX/1:	PC, BaseR	
ADDR2MUX/2:	ZERO offset6 PCoffset9 PCoffset11	;select the value zero ;select SEXT[IR[5:0]] ;select SEXT[IR[8:0]] ;select SEXT[IR[10:0]]
SPMUX/2:	SP+1 SP-1 Saved SSP Saved USP	;select stack pointer+1 ;select stack pointer-1 ;select saved Supervisor Stack Pointer ;select saved User Stack Pointer
MARMUX/1:	7.0 ADDER	;select ZEXT[IR[7:0]] ;select output of address adder
VectorMUX/2:	INTV Priv.exception Opc.exception	
PSRMUX/1:	individual settings, BUS	
ALUX/2:	ADD, AND, NOT, PASSA	
MIO.EN/1:	NO, YES	
R.W/1:	RD, WR	
Set.Priv/1:	0 1	;Supervisor mode ;User mode

LC-3 Control Architecture

Control FSM:
Design a FSM with
given state
diagram

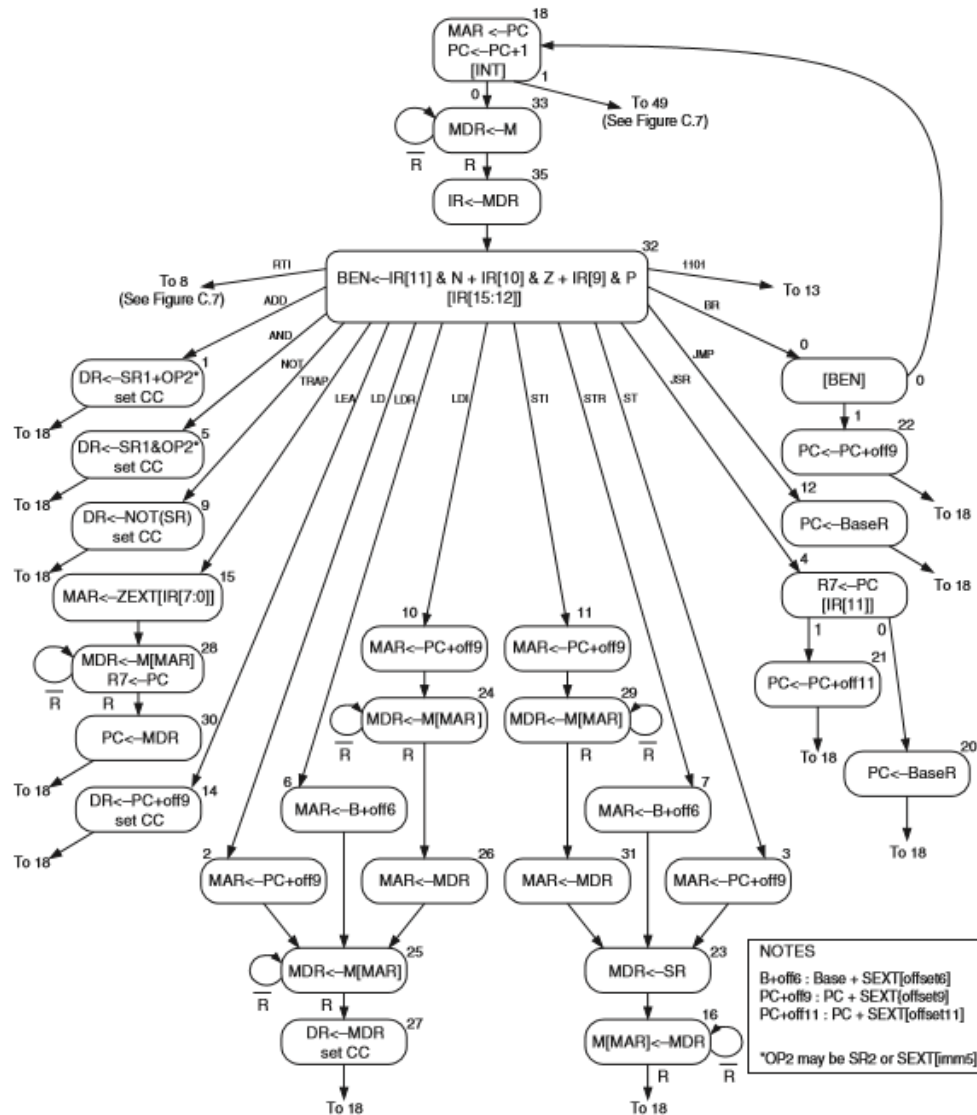


Figure C.2 A state machine for the LC-3

FSM Description

Instruction Fetch:

S18: $MAR \leftarrow PC$, $PC \leftarrow PC+1$,
If no INT, go to S33




To implement

$MAR \leftarrow PC$ needs: **GatePC = 1, LD.MAR = 1,**

$PC = PC+1$ needs: **PCMUX select PC+1, LD.PC = 1**

For each state

 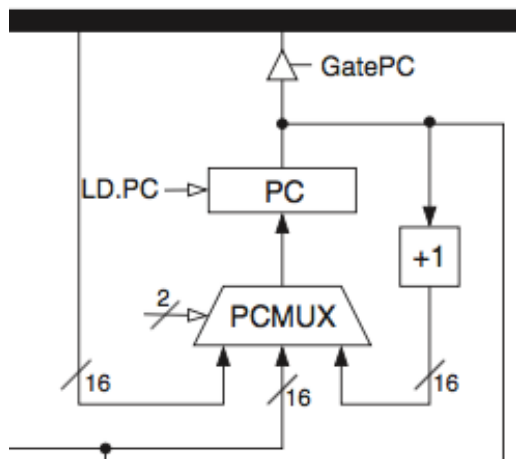 - activate or select appropriate Control signals
- Go to appropriate next state



Example: ST instruction

Instruction Fetch:

S18: MAR<-PC, PC<-PC+1, If no INT, goto S33

S33: MDR<-M, if R goto 35

S35: IR<- MDR, goto 32

Decode:

S32: BEN = [IR[11] & N+IR[10] & Z+IR[9] & P[IR[15:12]]] go to specific state

Evaluate address:

S3: MAR<- PC + off9 , goto 23



Fetch Operand:

S23: MDR<-SR, goto 16

Store result:

S16: M[MAR] <- MDR, If R goto S18

  As you can see some instructions need fewer cycles.



Processor Design Homework

You need to design a tiny processor with a given ISA.

- **Design the Data Flow part**
 - We will do that for you.
- **Identify the control signals needed**
 - We will do that for you.
- **Describe the sequential behavior using RTL/state diagram**
 - We will do that too.
- **Design the controller as a finite state machine**
 - Flip-flops to hold the state
 - Logic to generate control signals and to go to the next state
- **Construct, simulate and validate your design**

Control Design options

Hardwired control:

- Design the FSM using any hardware and optimize it.
- Large combinational blocks are usually designed using a PLA.
- Approach came back into vogue with RISC philosophy.

Microprogrammed control

- Fixed structure with a microsequencer
- Control signals stored in a ROM (or PROM)
- Control design then becomes “writing microinstructions”
- Changing/adding design easier, was popular at a time.

Modern processors use Verilog/VHDL specification automating part of the design.

- CSU was a major research center on Microprogramming for several years.
- I was personally responsible for dropping the term “Microprogramming” for the major international [meeting](#) in Dublin as chair of IEEE CS TC-Micro.

Control Design for Parallel processors

Pipelining

- Multiple instructions active at the same time
- An instructions is finishing, some partly done and a new one being fetched.
- Control signals for several instructions active at the same time!

Superscalar Processors:

- Multiple instructions are being fetched at a single time.

Simultaneous Multithreading Processors:

- Hardware supports multiple threads running at the same time in a single processor.

Multicore Processors:

- Each core has its own control unit.