

Fault Tolerant Computing

CS 530

Lecture Notes 2

Digital Systems: overview



Yashwant K. Malaiya
Colorado State University

Colorado State University, Fort Collins, Co

Digital Systems: overview

- Building blocks
- Combinational design & analysis
- **Untestable** faults
 - some faults are untestable due to redundancy
- Storage elements
- Finite state machines: sequential circuits
- **Testing** a block
 - How can a combinational of sequancial block be exercised to test for potential faults?


This is largely a review, but there are some new concepts in it.

Digital Systems: Overview


- **Building block hierarchy**
 - Subsystems (processors etc)
 - Combinational blocks, registers
 - Gates, storage elements
 - Switches (transistors)
- **Blocks can be**
 - Combinational (no memory)
 - Sequential (with states)

Combinational Blocks

 - Boolean functions without storage capability



 Truth table
Karnaugh maps
(minimization)
Algebraic description
Circuit diagram
(implementation)




If you have not seen Karnaugh maps before, you can find it in a textbook or on the web.

Circuit Minimization using Boolean Algebra

- Boolean logic lets us reduce the circuit

$$\begin{aligned} - X &= A'B'C' + A'BC' + ABC' + ABC = \\ &= A'C' + AB \end{aligned}$$
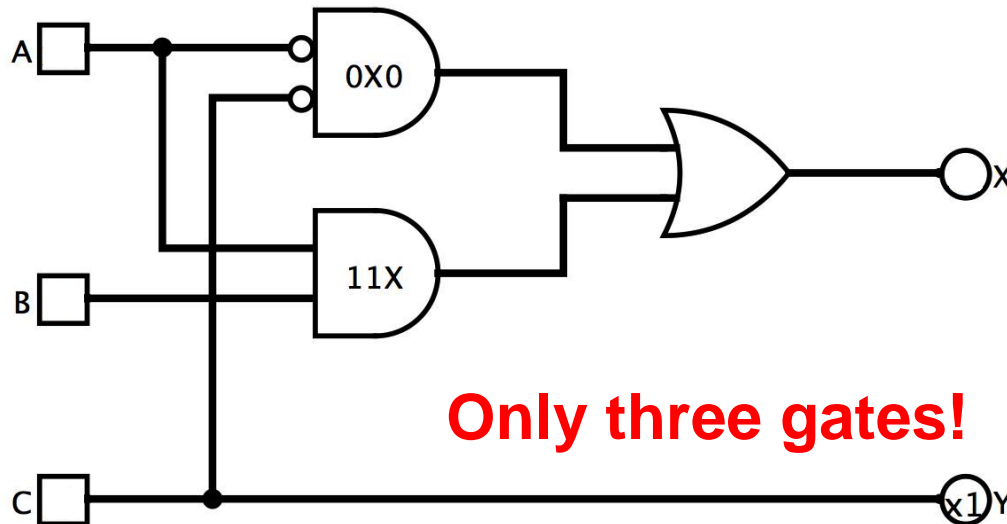
$$\begin{aligned} - Y &= A'B'C + A'BC + AB'C + ABC \\ &= A'C + AC = C \end{aligned}$$



A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

Try with Logisim!

Karnaugh maps to minimize literals

Based on set-theory

- Visual representation of algebraic functions
- Allow algorithmic minimization of boolean functions in sum-of-products form
- “adjacent” terms can be combined.
 - Adjacent: differ in one variable, complemented in one, not complemented in the other.

Example:

- $ABC + ABC' = AB(C + C') = AB$
- Thus ABC and ABC' are two pieces of AB .

Combining Minterms

- For n -variables, there are 2^n minterms, corresponding to each row of truth table.
- Some of them can be combined into groups of 2, (or 4 or 8 ..) to simplify the function.

Karnaugh Maps

Visual representation of algebraic functions to make it easy to spot “adjacent” minterms”

- Columns arranged so that *adjacent terms* are visually adjacent.
- Identify groups of 2, 4, 8 etc. terms that can be combined.
- All 1’s must be covered.
- A 1 can be used more than once, if needed.
- Sometimes the solution is not unique
- Next: maps for $X(A,B,C)$ and $Y(A,B,C)$

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

Karnaugh Maps: Visualization of algebra

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

K Map for X

B

A\BC	00	01	11	10
0	1	0	0	1
1	0	0	1	1

C

A

K Map for Y

B

A\BC	00	01	11	10
0	0	1	1	0
1	0	1	1	0

C

A

Karnaugh Maps: Visualization of algebra

		B				
A\BC		00	01	11	10	
0	1	0	0	1		
1	0	0	1	1	A	
		C				

		B				
A\BC		00	01	11	10	
0	0	1	1	0		
1	0	1	1	0	A	
		C				

X: $A'B'C' + A'BC' = A'C'$; $ABC + ABC' = AB$

Y: $A'B'C + A'BC + AB'C + ABC = A'C + AC = C$

Thus minimized function is

$$X = A'C' + AB \quad Y = C$$

4-variable Kmaps / Design

		<u>C</u>			
		00	01	11	10
A	00	1			1
	01		1		
	11				
	10	1			1
		<u>D</u>			

$$F(A,B,C,D) = ABC' + A' C' D + A' BC + ACD + ?$$

$$F(A,B,C,D) = B' D' + \underline{\hspace{2cm}}$$

		<u>C</u>			
		00	01	11	10
A	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	
		<u>D</u>			

Try them with Logisim

4-variable Kmaps / Design

		C			
		00	01	11	10
A	00	1			1
	01		1		
	11				
	10	1			1
		D			

$$F(A,B,C,D) = ABC' + A' C' D + A' BC + ACD \quad \text{+?}$$


$$F(A,B,C,D) = B' D' + A' BC' D$$

		C			
		00	01	11	10
A	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	
		D			

Try them with Logisim

Combinational Example

x1	x2	x3	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


Implementation A

$$F = x1'x2 + x1x3'$$

Implementation B

$$F = x1'x2 + x1x3' + x2x3'$$

 

redundant

Note that the $x2x3'$ term is redundant.
Here a prime indicates complement.

A stuck-at-0 fault makes the line always stay at 0 regardless of what it is supposed to be.


Special Considerations

- In a redundant design, a fault may be undetectable.
- Undetectable faults are a major problem in testing.


in software also

Fan-out: one output feeding multiple inputs.

Fan-out

 

Reconvergent fan-out

 


Reconvergent fan-out can lead to problem in testing, as we will see later.

Storage Elements

- Synchronized by *clock* or *write* signals
- Construction: static (flip-flop), dynamic (capacitative, need refreshing)
- Functional: single input (D-type), double input
- Timing: rising or falling edge triggered
Pulse type etc
- Significant instants:
 - when input is sampled
 - when outputs are influenced

Ex: Rising Edge D flipflop

 


Samples on rising edge
Output influenced soon after

Q_t	D	Q_{t+1}
0	0	0
0	1	1
1	0	0
1	1	1



During sampling
input must remain
stable

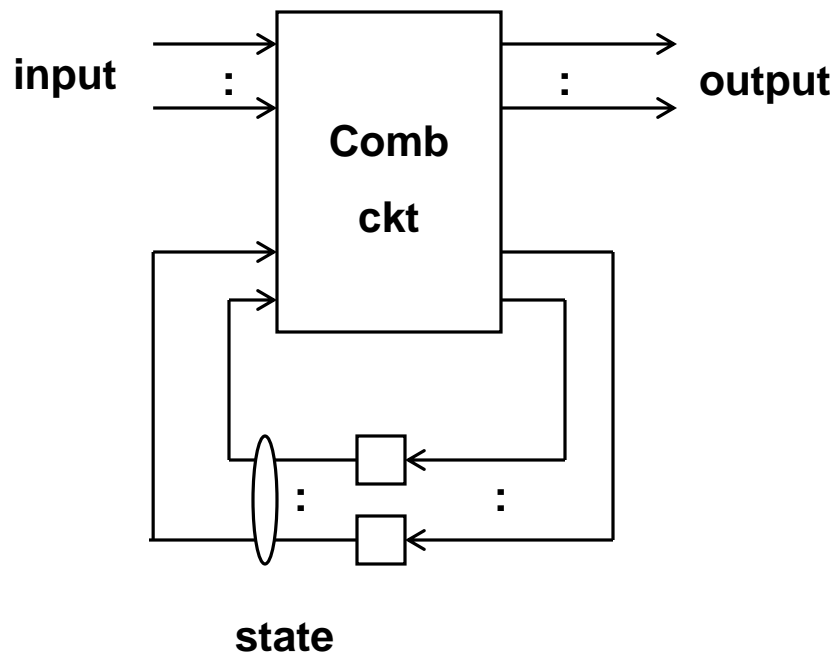Sequential Circuits are Finite State Machines(FSMs)




- **Next state = $N(\text{state}, \text{input})$**
- **Output = $Z(\text{state}, \text{input})$**

FSM Description

state	Input x	
	0	1
1	2,1	3,0
2	2,1	4,0
3	1,0	4,0
4	3,1	3,0

Entries: N,Z

 

Format:
x/z

input

state

output

0	1	0
1	2	4
1	0	1

Based on FSM state table

(or state diagram)

Digital System with functional blocks

- **Ex: a microprocessor**

Blocks are

- **Paths**
 - Signals, buses, nets
- **Combinationals**
 - Random logic, PLA, ROM
- **Sequential**
 - Flipflps, registers, memory arrays
 - Finite state machines (control part)
- **System design objectives**
 - functionality, reliability, peformence

Exercising a block

- **Combinational blocks:** a *test-vector* (or pattern) applied at a time for testing.
 - Exception: when testing for delay faults
- **Sequential:** a *test-sequence* (a sequence of input vectors) at a time with proper initialization.

References

- See any Logic Design text-book for combinational and sequential circuits and Karnaugh Maps. For example: Computer System Architecture by Morris Mano.
- Karnaugh Maps:
<http://web.archive.org/web/20080819230843/http://www.cs.usm.maine.edu/~welty/karnaugh.htm>
- Design for Testability in Digital Integrated circuits, Bob Strunz, Colin Flanagan, Tim Hall, Article, locally available at http://www.cs.colostate.edu/~cs530/digital_testing.pdf