

Fault Tolerant Computing

CS 530

Testing Sequential Circuits

Yashwant K. Malaiya
Colorado State University

Why Testing Sequential Circuits is Hard

- **To test a sequential circuit we need to**
 - Initialize it into a known state (reset it: it's easy)
 - Apply a test sequence to it long enough to
 - Sensitize the fault
 - Propagate the error to output
 - Both can take many clock cycles
 - For n flip-flops, there are 2^n states, but these can occur in different order, causing numerous possible sequences.
- **Common Approach: reduce the problem to that of combinational testing**

Outline

- **Sequential circuits without feedback**
 - BIST
- **Sequential circuits with feedback**
 - DFT: scan
 - Extended D-algorithm (mention only)
 - Functional testing of FSMs
 - Initialization problem
- **Incremental testing for complex systems**

Note that FSM (finite state machine) testing concepts are applicable to both hardware sequential circuits and software that has “states”.

Testing Sequential Circuits

- In general need to test for both
 - Functionality (examined here)
 - Timing (components too slow, too fast, not synchronized)
- Parts of a sequential circuit:
 - **Combinational logic:** faults: stuck 0/1, delay
 - **Flip-flops:** faults: input, output stuck 0/1, delay
no latch 0/1 capability


Malaiya, & Narayanaswamy, "*Testing for Timing Faults in Synchronous Sequential Integrated Circuits*," Intl. Test Conf., 1983.

Alassadi, Malaiya & Jayasumana, "Faulty Behavior of Storage Elements and its Effects on Sequential Circuits" IEEE Trans. VLSI Systems, Dec. 1993

Two common cases that simplify testing

- **When the combinational logic is sandwiched between two registers, and there is no feedback**
 - Problem reduced to testing the combinational logic
 - Many faults in flip-flops are equivalent to faults in the combinational logic, thus faults in flip-flops can be ignored for simplification.
- **When there is feedback, but during testing feedback can be disabled when needed**
 - Scan approaches

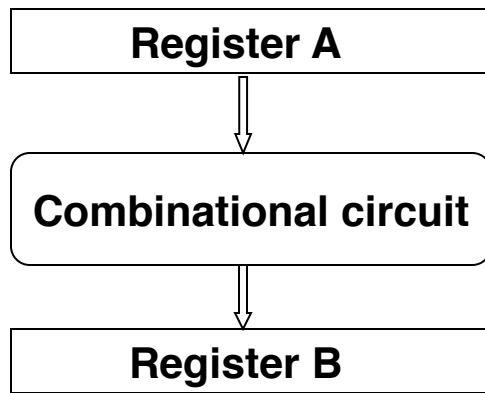Testing Sequential circuits without feedback




- 1. Generate test vectors for the combinational circuit.**
- 2. Place a vector in A**
- 3. Examine response in B**
- 4. Steps 2,3 can be done using**
 - a. Machine instructions**
 - b. Microinstructions**
 - c. Specialized hardware**

Built-in Self-Test Approach

- Some registers can double as test pattern generators during testing.
- Some registers can also work as “signature analyzers” during testing
 - A Signature analyzer compresses a large number of output vectors into a single vector called “signature”.
- Well known designs for generators and signature analyzers are available.

The theory behind both generators and signature analyzers often involves “polynomial division” using “LFSRs (Linear feedback shift registers” , the same algorithm is used for calculating CRC in computer networks!

BIST (Built-in self-test)

 

ALFSR: autonomous linear feedback shift register.

Better generators include our **antirandom test generator.**


- **Generator generates **pseudorandom** vectors. Often an ALFSR.**
- **Signature analyzer compresses all successive responses into a signature. Usually an LFSR.**
- **Compared with **known good signature**.**
- **Aliasing probability: prob. that a bad circuit can result in good signature. Generally very small.**

Sequential Circuits with feedback

**Alexander cutting the
Gordian Knot**



Sequential Circuits with feedback

 


Some software programs are frequently tested as FSMs

 - **Example: processor control unit**
 - Input: status, opcode
 - Output: control lines
- **Structural testing issues:**
 - How to obtain a desired (x,y) vector
 - How to propagate error
- **Functional testing issues:**
 - Prove all transitions/outputs are correct

Sequential Circuits with feedback: Scan-chain approach

- **Design for testability:** feedback-less during testing. The flip-flops can be configured to form **scan-chains**.



- **Scan Design:** modes
 - **Normal mode:** parallel in/out
 - **Test mode:** serial in/out
- **Sequence of operations**
 - **Scan a vector:** test mode
 - **Latch response:** normal mode
 - **Scan response out:** test mode
- **If scan-chain too long**
 - **Use Multiple chain**
 - **Use Partial scan**

D-Algorithm: Sequential Circuits

- You can use D-algorithm for sequential circuits, but
 - It can be cumbersome to generate tests
 - Test application time can be very long
- See literature if you are interested. For example
[Test Generation for Sequential Circuits](#)

Sequential Circuit Initialization Problem

- **At power-up the state is undefined.**
- **How to get FSM in a known state?**
 1. **Applying an input sequence: theoretical importance only**
 2. **Resetting to an initial state**
- **Resetting always used in practice**
 - **using a reset/clear line**
 - **Computers: power-on sequence to initialize PC, SP, interface registers etc.**


Functional Testing of FSMs

- **Given:** state table **Objective:** confirm it is obeyed
- **Two alternative approaches:**
 1. **If the State is directly observable:**
 1. **Much easier**
 2. Use *Euler path*, if it exists, to minimize testing
 2. **Only outputs observable: “*Checking sequence*”**
 - a. Prove all states exist
 - b. For all inputs for each state, these are correct
 - Next state
 - Outputs
- **Theoretical, Complex and lengthy** (*see literature if interested*)

Testing Complex Systems

- A Complex system includes several **components**
- Approach:
 - Assume a **fault model** for each *component*
 - Assume a system model that takes into account interaction of components
- Design a testing strategy such that these are adequately tested
 - each individual component
 - Interaction of components
- A “**component**” may be a
 - Physical component
 - Segment of the functionality

Incremental Testing Approach

 

D Brahme, JA Abraham, Functional Testing of Microprocessors, IEEE Trans Comp, Jun 1984, pp. 475- 485.

- Partition system into **layers** such that layer i can be exercised using only layers $0, \dots, i-1$.
- Test components in each layer in the sequence L_0, L_1, \dots, L_n .
- Layering may require
 - Assumptions
 - Disabling feedback during testing
- Proofs of complete coverage can be constructed.
- Fault isolation can be done.

Incremental testing: Example: Processor Based systems

Sequence for testing:

- **Self-test processor:**
 - Basic instructions
 - Addressing modes
 - Complex instructions
- **Test Memory system and buses using processor**
- **Test I/O devices/ports**
- **Test peripheral devices**
- **Test software integrity**

References

- See earlier references in previous Lecture Notes.
- R. Dorofeeva, K. El-Fakih, S. Maag, A. R. Cavalli, N. Yevtushenko, **FSM-based conformance testing methods: A survey annotated with experimental evaluation**, Information and Software Technology, Volume 52, Issue 12, 2010, pp. 1286-1297.
- D Brahme, JA Abraham, **Functional Testing of Microprocessors**, IEEE Trans Comp, Jun 1984, pp. 475- 485.
- V.D. Agrawal, C.R. Kime, K.K. Saluja, **A Tutorial on Built-in Self-Test** Part 1: Principles. IEEE Design & Test January 1993, Pages: 73 - 82 Part 2: Applications, IEEE Design & Test April 1993, pp. 69 - 77.
- C-C. Liaw, S. Y. Su, and Y. K. Malaiya. **"Test generation for delay faults using stuck-at-fault test set."** Proc. of International Test Conf. 1980, pp. 167-175